

CART360
Etude Four: EmitEmo
Aniesha Sangarapillai

Links:

Class Website: <http://anieshadesigns.com/cart360/etudes.html>

Github: https://github.com/Aniesha08/cart360/tree/master/Etudes/Etude_4

PART 1 - Documentation

To create the circuit, I had used 10Ω resistors for the mode & keyboard buttons as well as for the photocell. For the RGB led light, I had used a 200Ω resistor. One of the biggest issues that I found was that my mode button LED would not stay in one stable color when selecting the modes. I had spent so much time trying to figure out what may be the issue. I consulted Zahra and we figured out that I had connected my resistor in the same row as the bottom row of my mode button instead of connecting in the same row as the cable connecting to pin 2.



